


BJT DC-Biasing

Engr. Raymond J. Pidor, PECE



Operating Point

- ▶ Biasing – the term for the application of dc voltages to establish a fixed level of current and voltage
- ▶ For transistor amplifiers, the resulting dc current and voltage establish an operating point on the characteristics that define the region that will be employed for amplification of the applied signal.
- ▶ Since the operating point is a fixed point on the characteristics, it is also called the quiescent point (abbreviated Q-point)

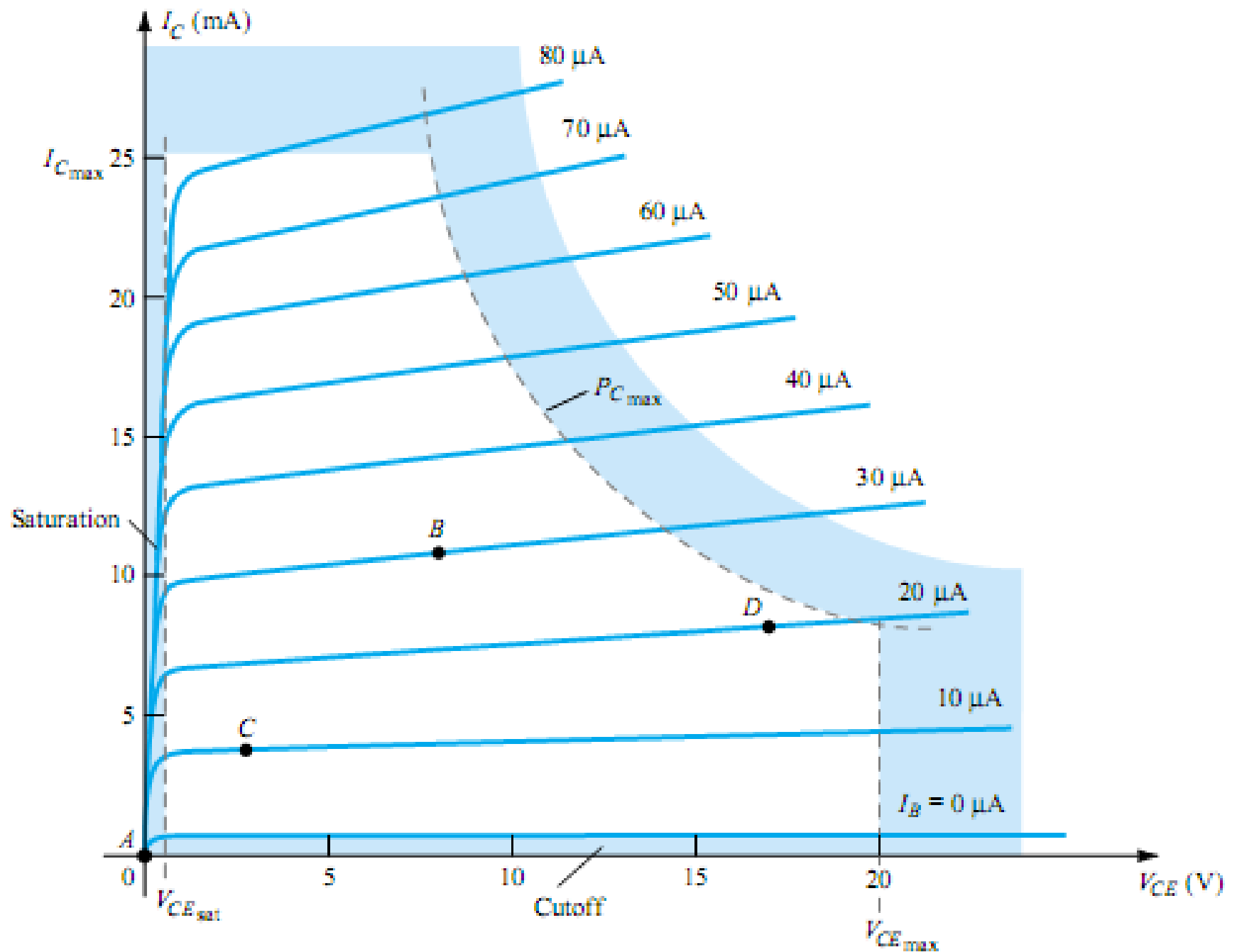


BJT biased in linear/active region

- ▶ The base-emitter junction must be forward-biased (p-region voltage more positive), with a resulting forward-bias voltage of about 0.6 to 0.7 V.
- ▶ The base-collector junction must be reverse-biased (n-region more positive), with the reverse-bias voltage being any value within the maximum limits of the device.



Mode of Operations

- ▶ Linear region
 - Base–Emitter junction is forward biased
 - Base–Collector junction is reverse biased
- ▶ Cut–off region
 - Base–Emitter junction is reverse biased
- ▶ Saturation region
 - Base–Emitter junction is forward biased
 - Base–Collector junction is forward biased

Fixed-Bias

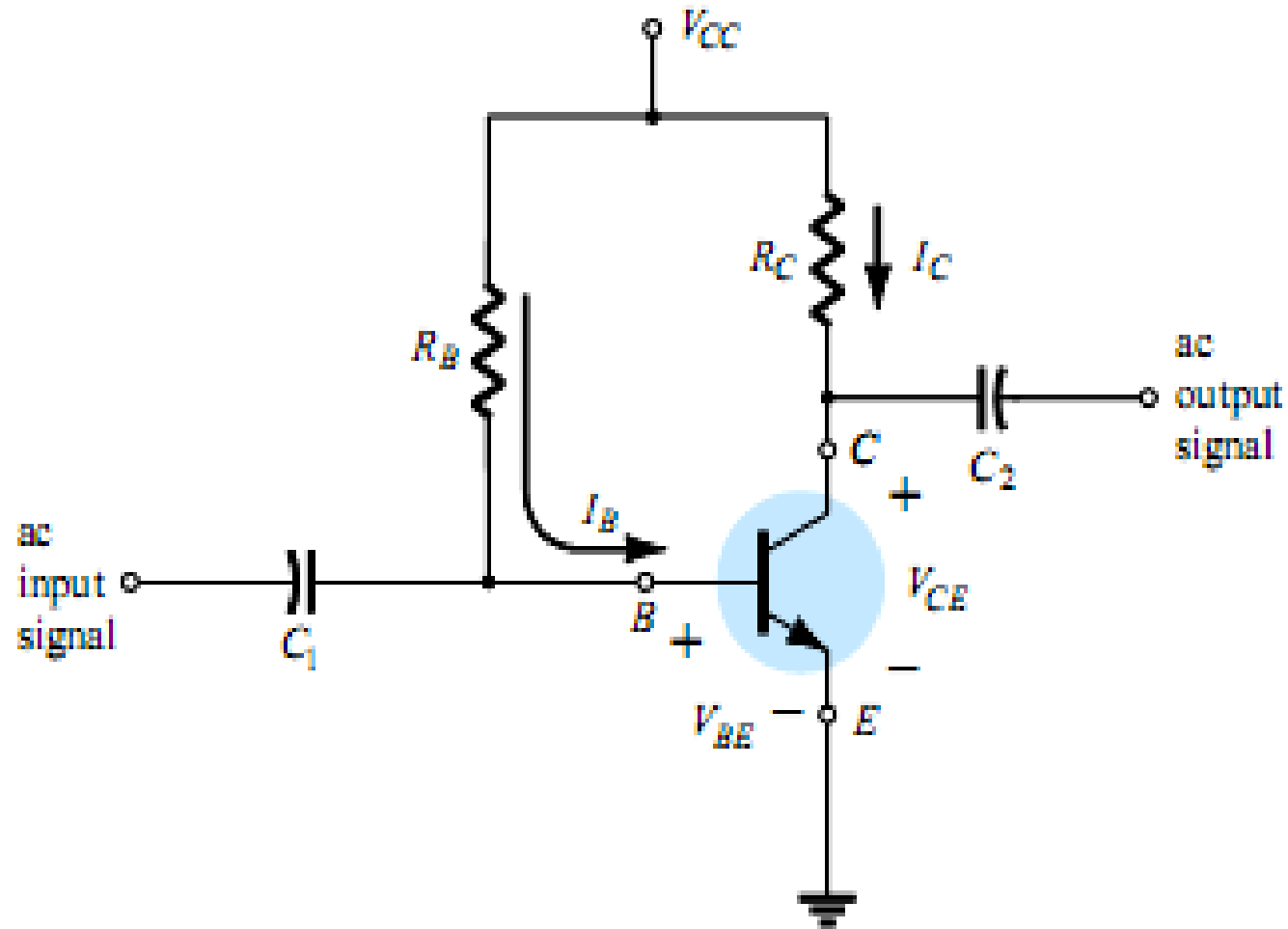


Input Side

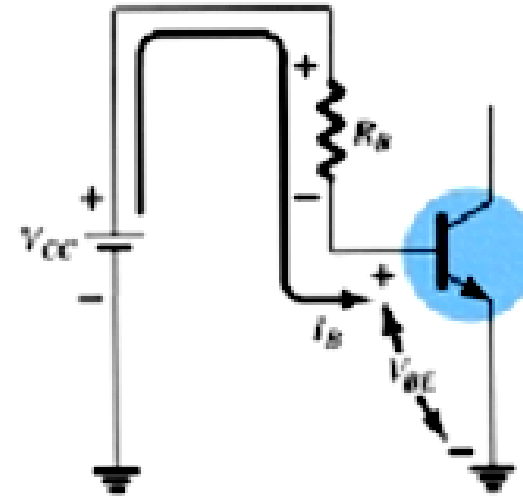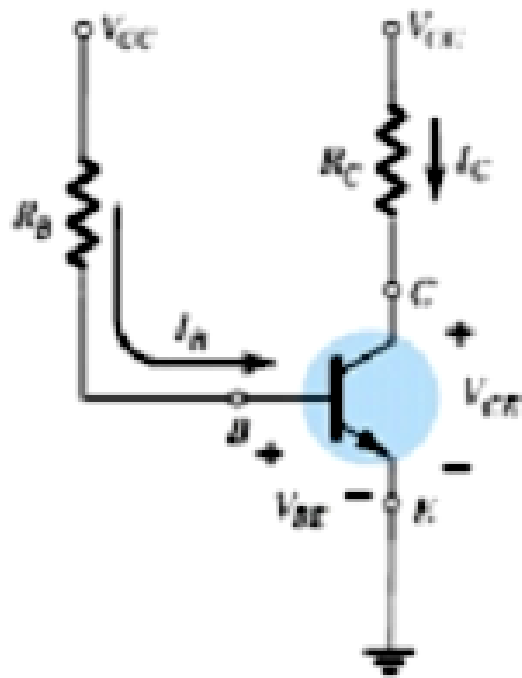

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

Output Side

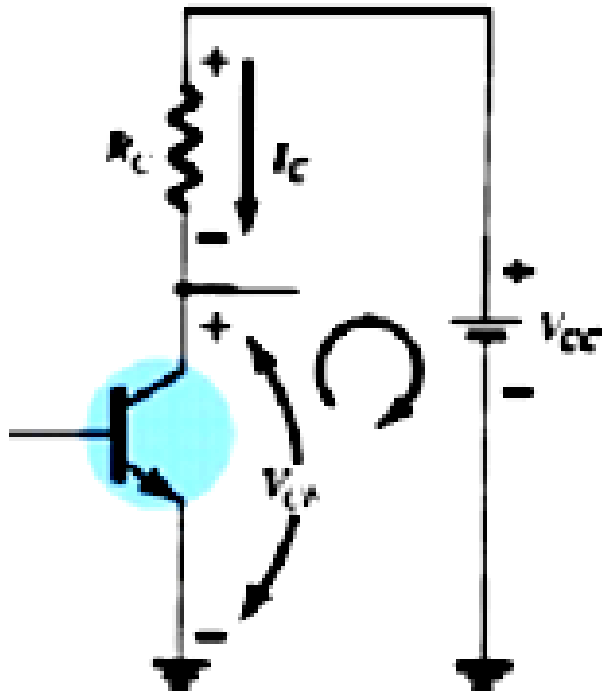

$$I_C = \beta I_B$$

$$V_{CE} + I_C R_C - V_{CC} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$



$$V_{CE} = V_C - V_E$$

$$V_{CE} = V_C$$

$$V_{BE} = V_B - V_E$$


$$V_{BE} = V_B$$

Loadline

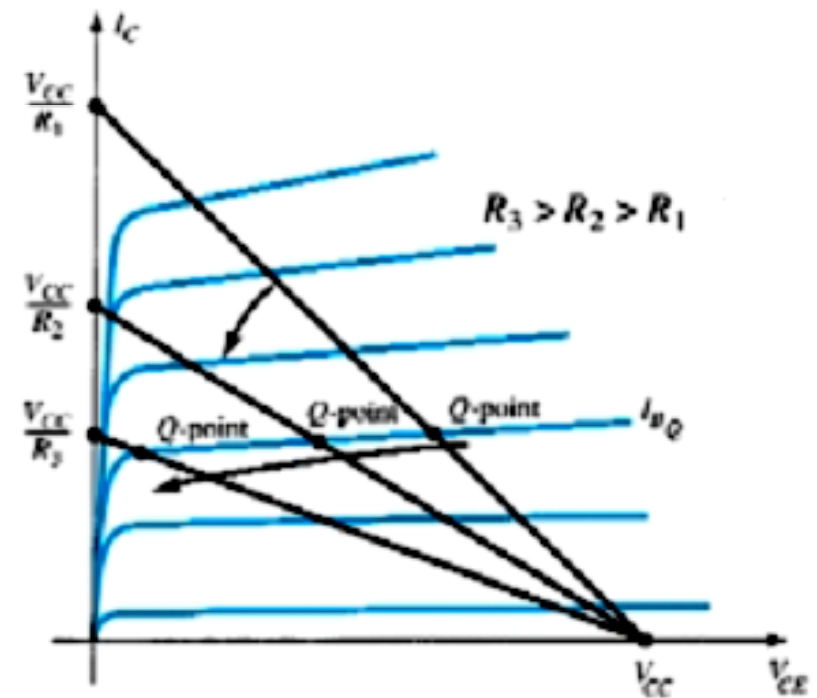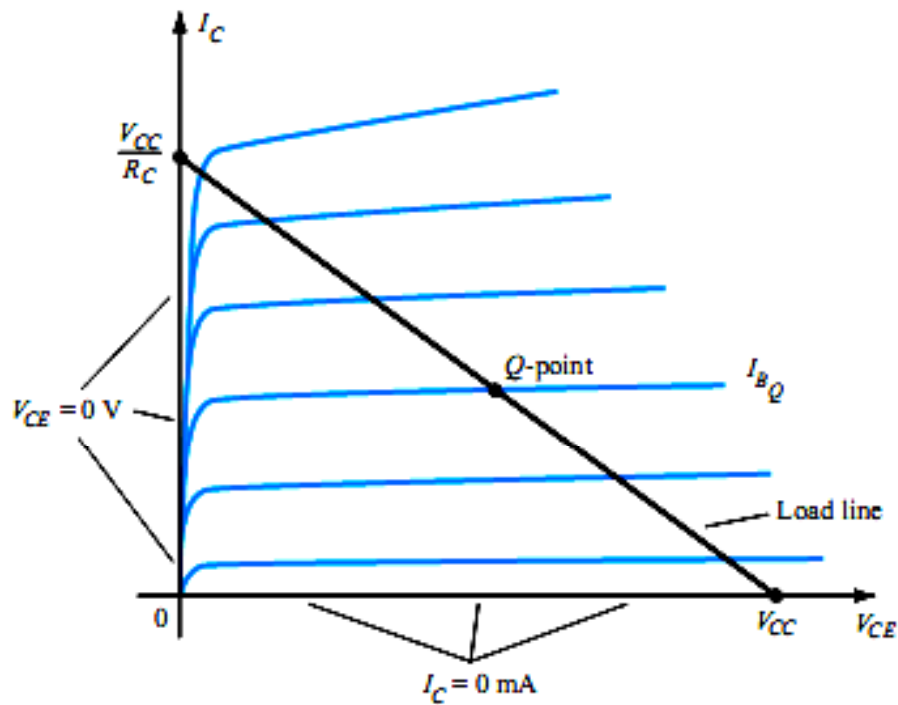

Prob:

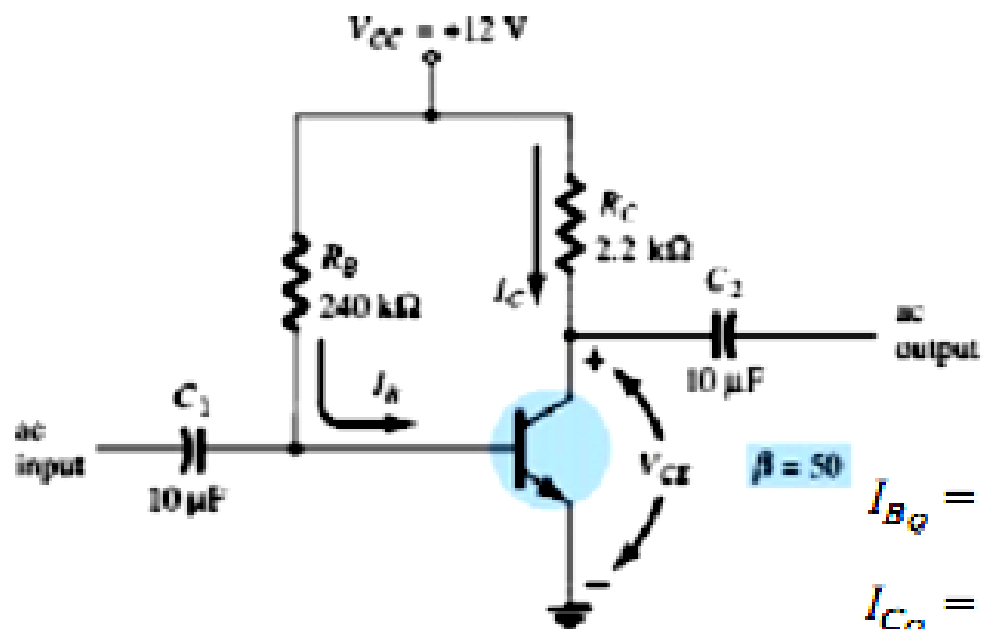- Determine I_{BQ} , I_{CQ} and V_{CEQ} .




$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{240 \text{ k}\Omega} = 47.08 \mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = (50)(47.08 \mu\text{A}) = 2.35 \text{ mA}$$


$$\begin{aligned} V_{CEQ} &= V_{CC} - I_C R_C \\ &= 12 \text{ V} - (2.35 \text{ mA})(2.2 \text{ k}\Omega) \\ &= 6.83 \text{ V} \end{aligned}$$

Seatwork:

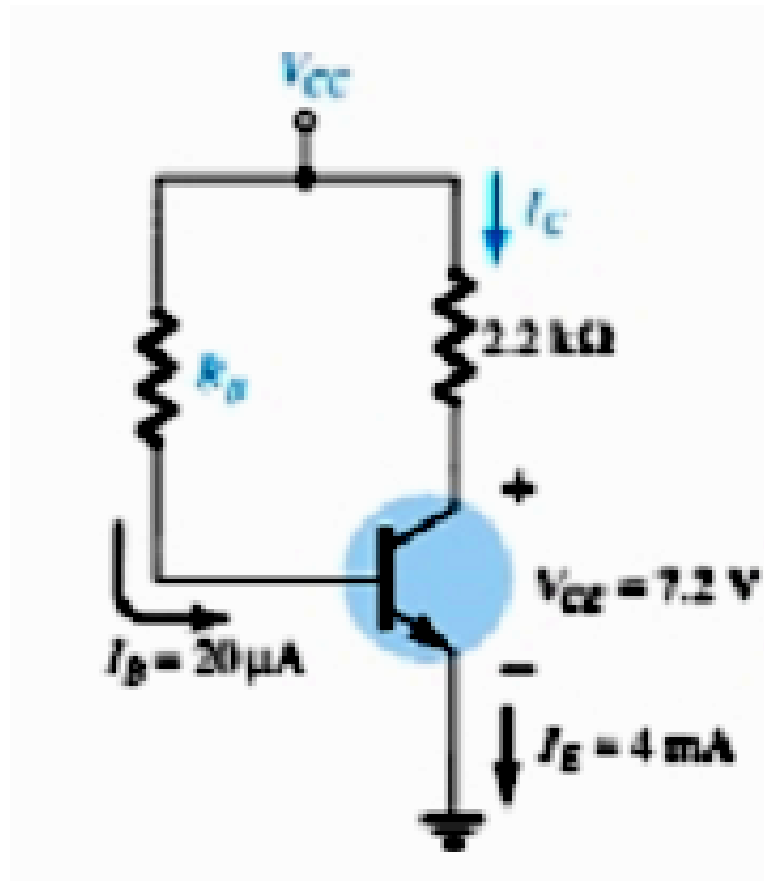
- ▶ Determine I_C , V_{CC} , β , and R_B .



Emitter-Stabilized Bias

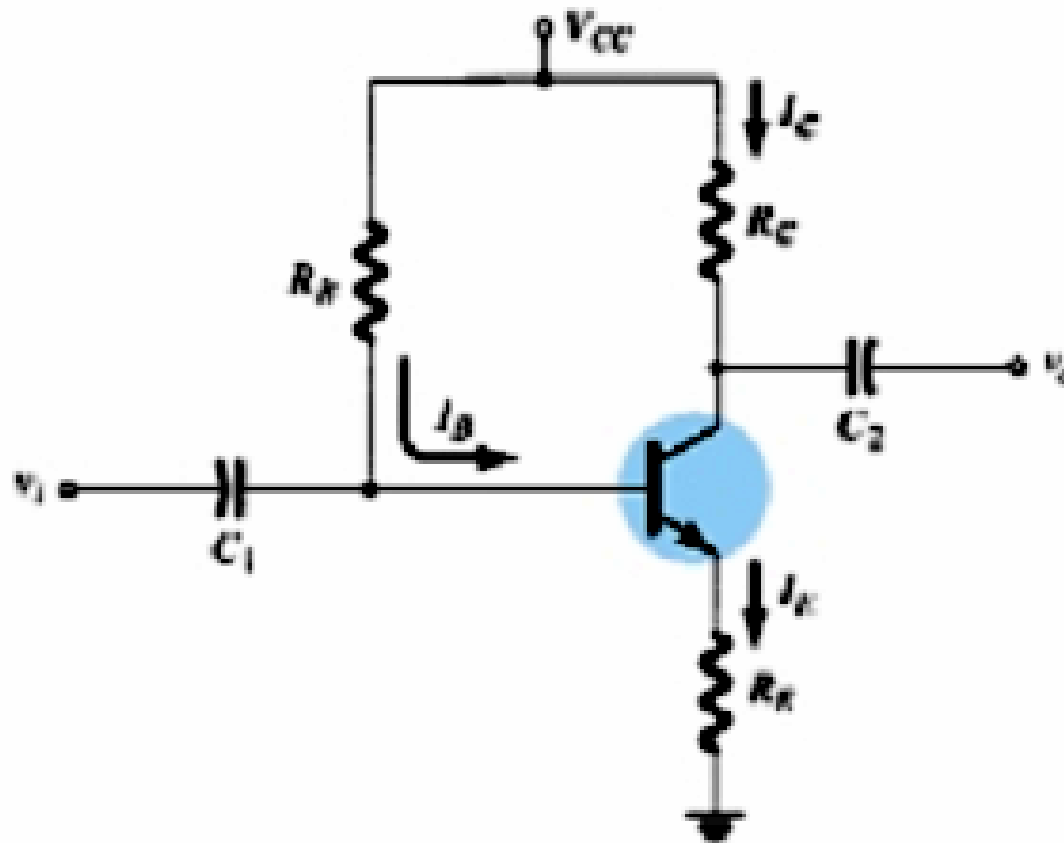

Input Side

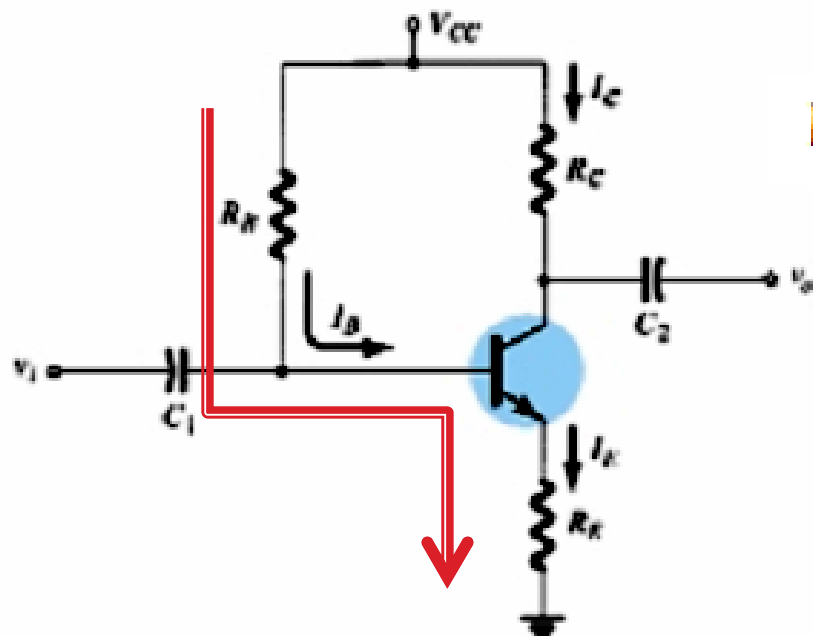


$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

$$I_E = (\beta + 1)I_B$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$

Output Side

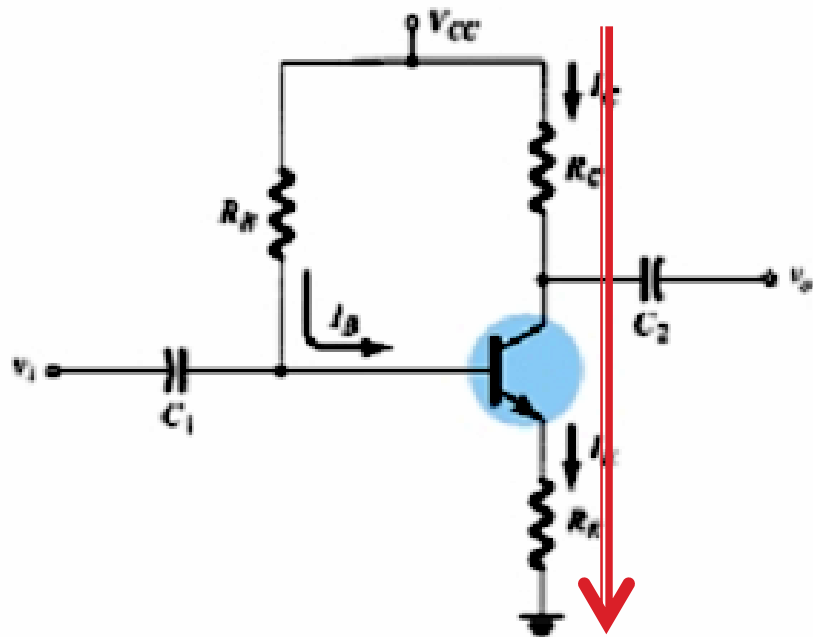

$$V_{CE} - V_{CC} + I_C(R_C + R_E) = 0$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$


$$V_E = I_E R_E$$

$$V_{CE} = V_C - V_E$$

$$V_C = V_{CE} + V_E$$


$$V_C = V_{CC} - I_C R_C$$

Loadline

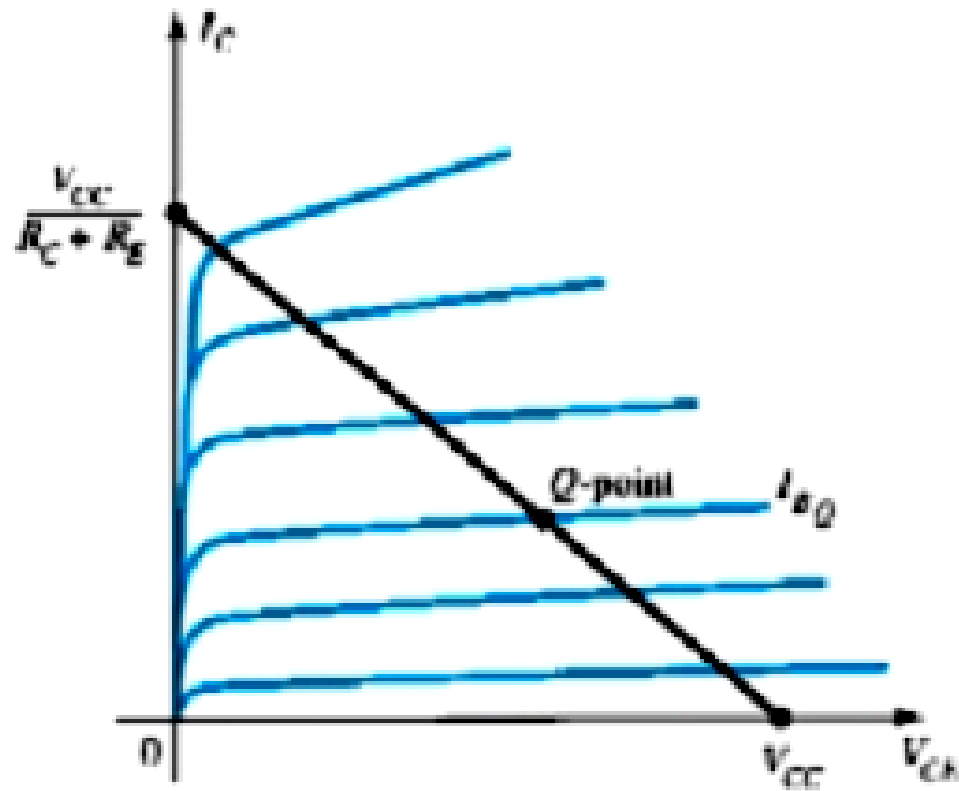

Problem:

- Determine I_B , I_C , V_{CE} and V_C .

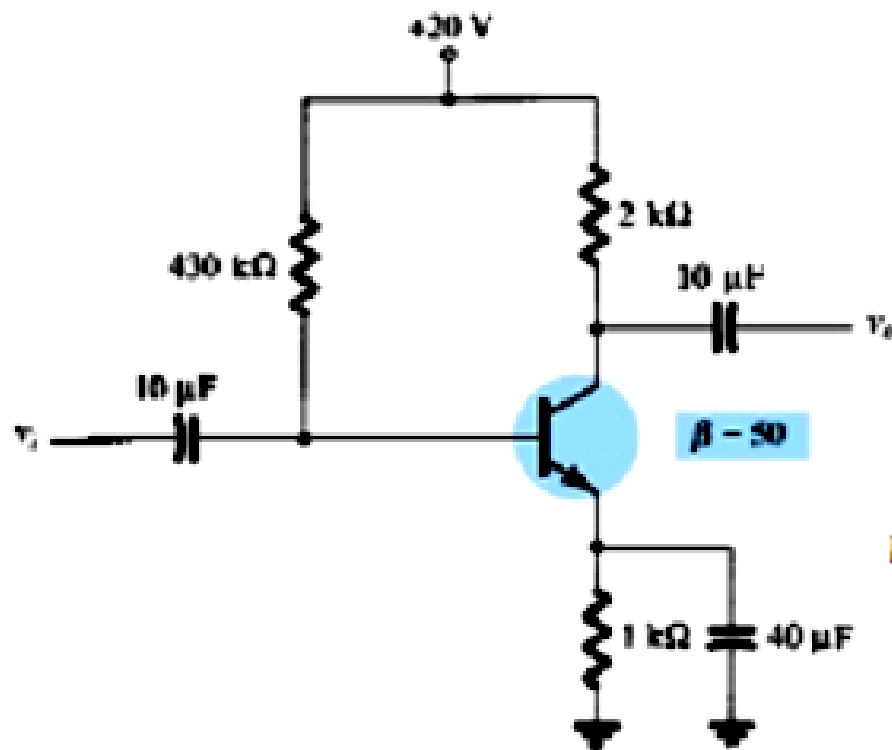

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{20 \text{ V} - 0.7 \text{ V}}{430 \text{ k}\Omega + (51)(1 \text{ k}\Omega)}$$

$$= \frac{19.3 \text{ V}}{481 \text{ k}\Omega} = 40.1 \mu\text{A}$$

$$I_C = \beta I_B$$

$$= (50)(40.1 \mu\text{A})$$

$$\cong 2.01 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

$$= 20 \text{ V} - (2.01 \text{ mA})(2 \text{ k}\Omega + 1 \text{ k}\Omega) = 20 \text{ V} - 6.03 \text{ V}$$

$$= 13.97 \text{ V}$$


$$V_C = V_{CC} - I_C R_C$$

$$= 20 \text{ V} - (2.01 \text{ mA})(2 \text{ k}\Omega) = 20 \text{ V} - 4.02 \text{ V}$$

$$= 15.98 \text{ V}$$


Seatwork:

- Determine β , V_{CC} and R_B .

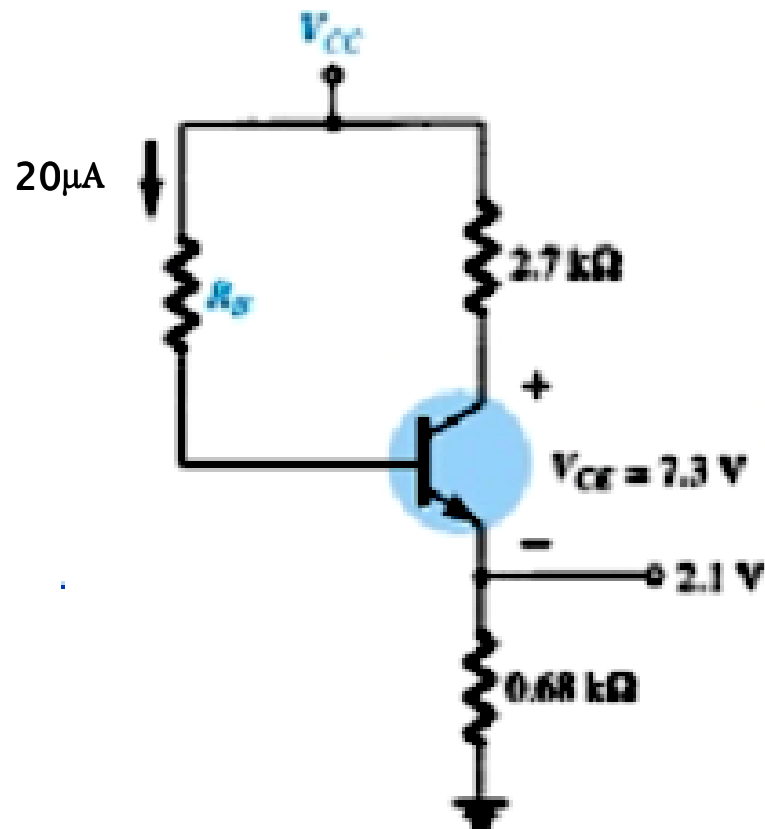


Voltage-Divider Bias


- ▶ Exact Analysis

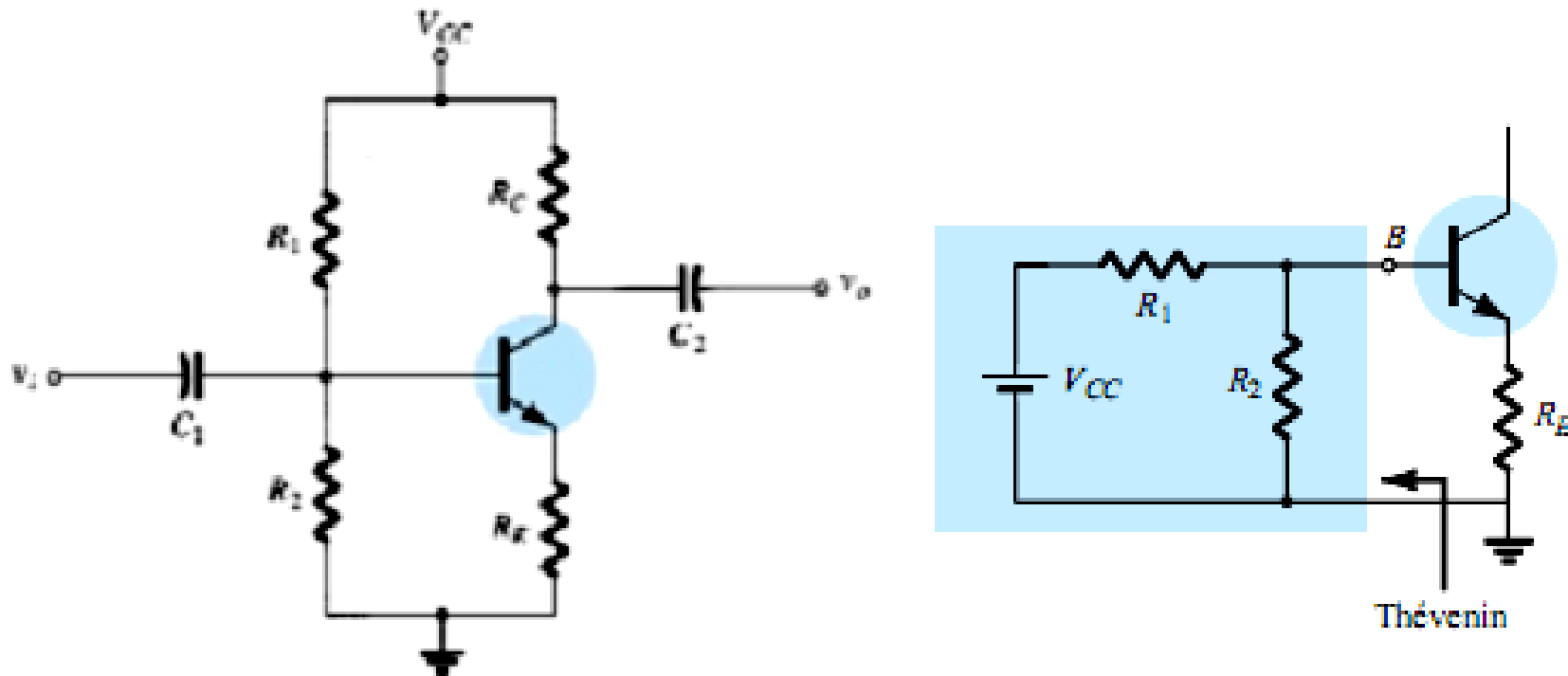

R_{Th} and E_{Th}

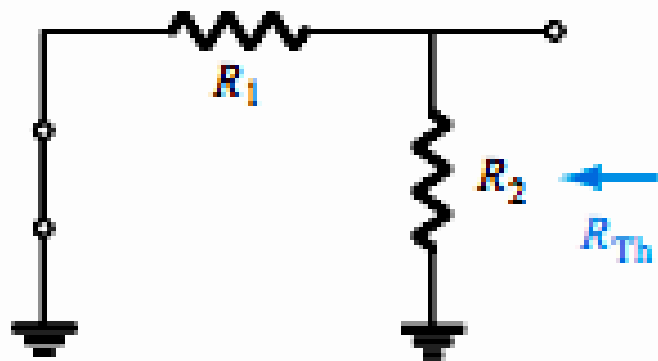


$$R_{Th} = R_1 \parallel R_2$$

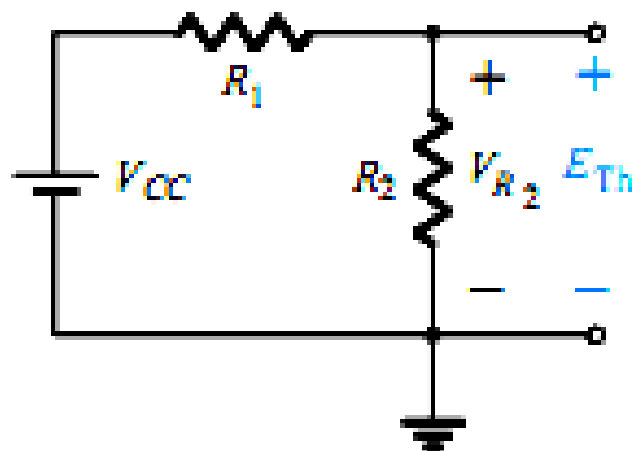


$$E_{Th} = V_{R_2} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

Thevenin's Circuit

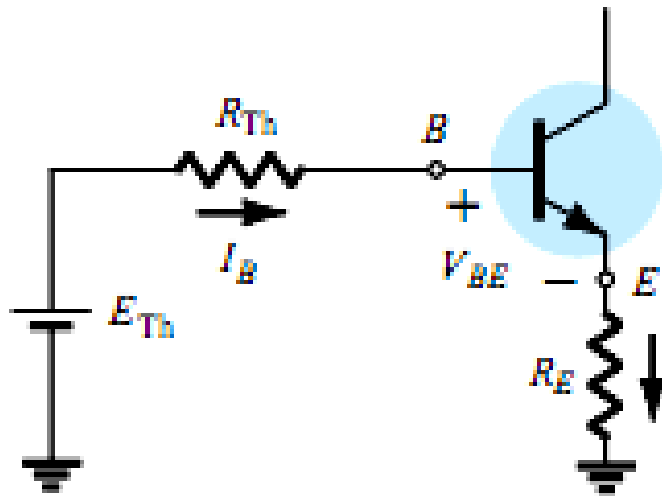

$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E}$$

Output Side

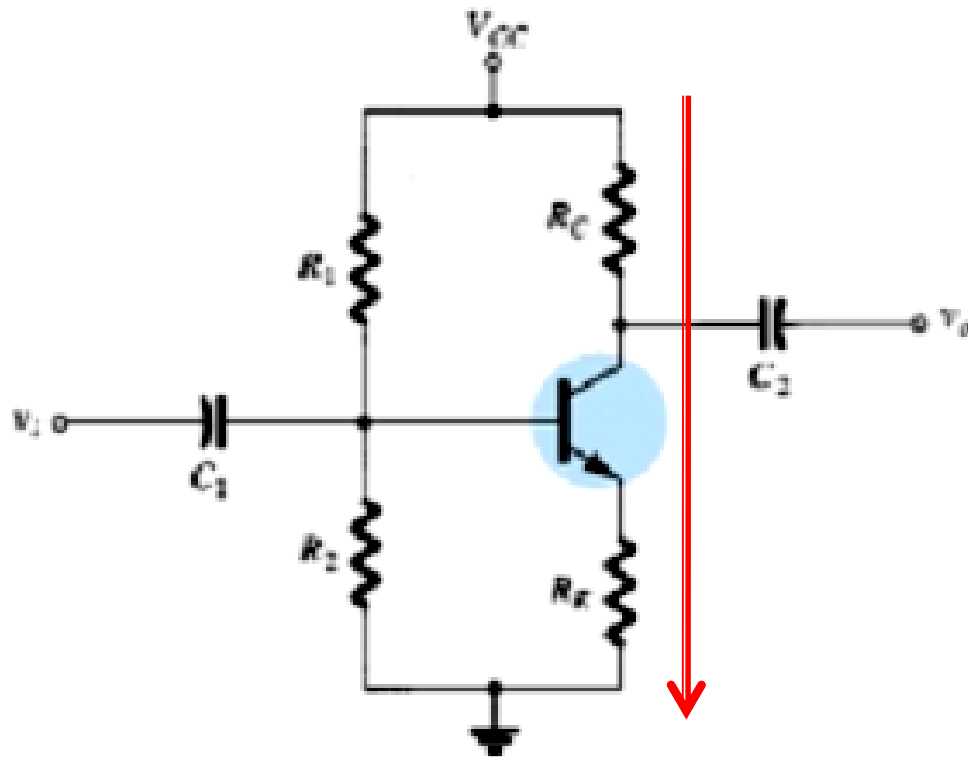

$$V_{CE} - V_{CC} + I_C(R_C + R_E) = 0$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

$$V_E = I_E R_E$$


$$V_{CE} = V_C - V_E$$

$$V_C = V_{CE} + V_E$$

$$V_C = V_{CC} - I_C R_C$$

Problem:

- Determine I_C and V_{CE} .

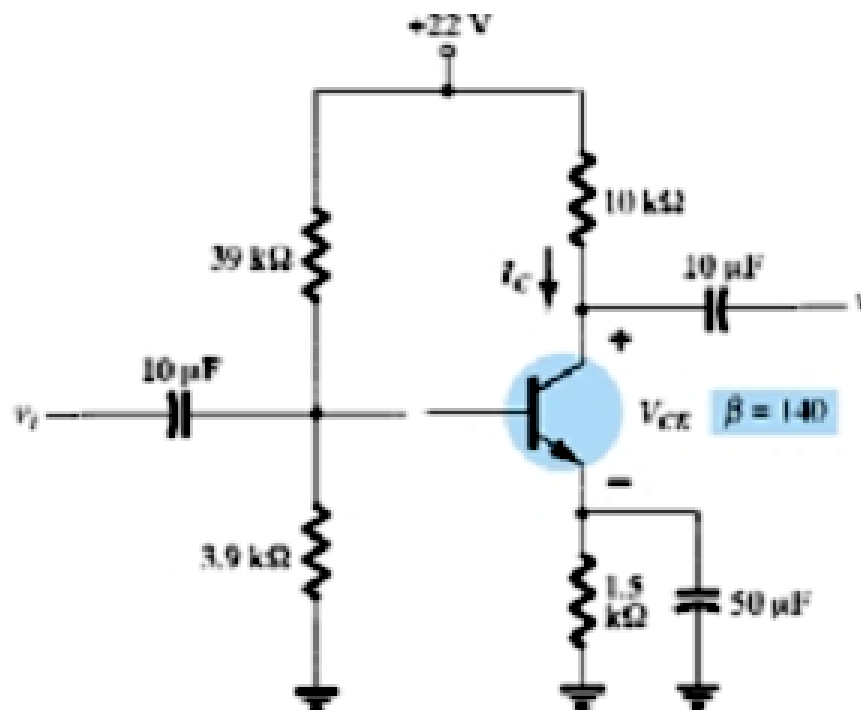

$$R_{Th} = R_1 \parallel R_2$$

$$= \frac{(39 \text{ k}\Omega)(3.9 \text{ k}\Omega)}{39 \text{ k}\Omega + 3.9 \text{ k}\Omega} = 3.55 \text{ k}\Omega$$

$$E_{Th} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$= \frac{(3.9 \text{ k}\Omega)(22 \text{ V})}{39 \text{ k}\Omega + 3.9 \text{ k}\Omega} = 2 \text{ V}$$

$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E}$$

$$= \frac{2 \text{ V} - 0.7 \text{ V}}{3.55 \text{ k}\Omega + (141)(1.5 \text{ k}\Omega)} = \frac{1.3 \text{ V}}{3.55 \text{ k}\Omega + 211.5 \text{ k}\Omega}$$

$$= 6.05 \text{ }\mu\text{A}$$

$$I_C = \beta I_B$$

$$= (140)(6.05 \text{ }\mu\text{A})$$

$$= \mathbf{0.85 \text{ mA}}$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$


$$= 22 \text{ V} - (0.85 \text{ mA})(10 \text{ k}\Omega + 1.5 \text{ k}\Omega)$$

$$= 22 \text{ V} - 9.78 \text{ V}$$

$$= \mathbf{12.22 \text{ V}}$$

Voltage-Divider Bias

- ▶ Approximate Analysis

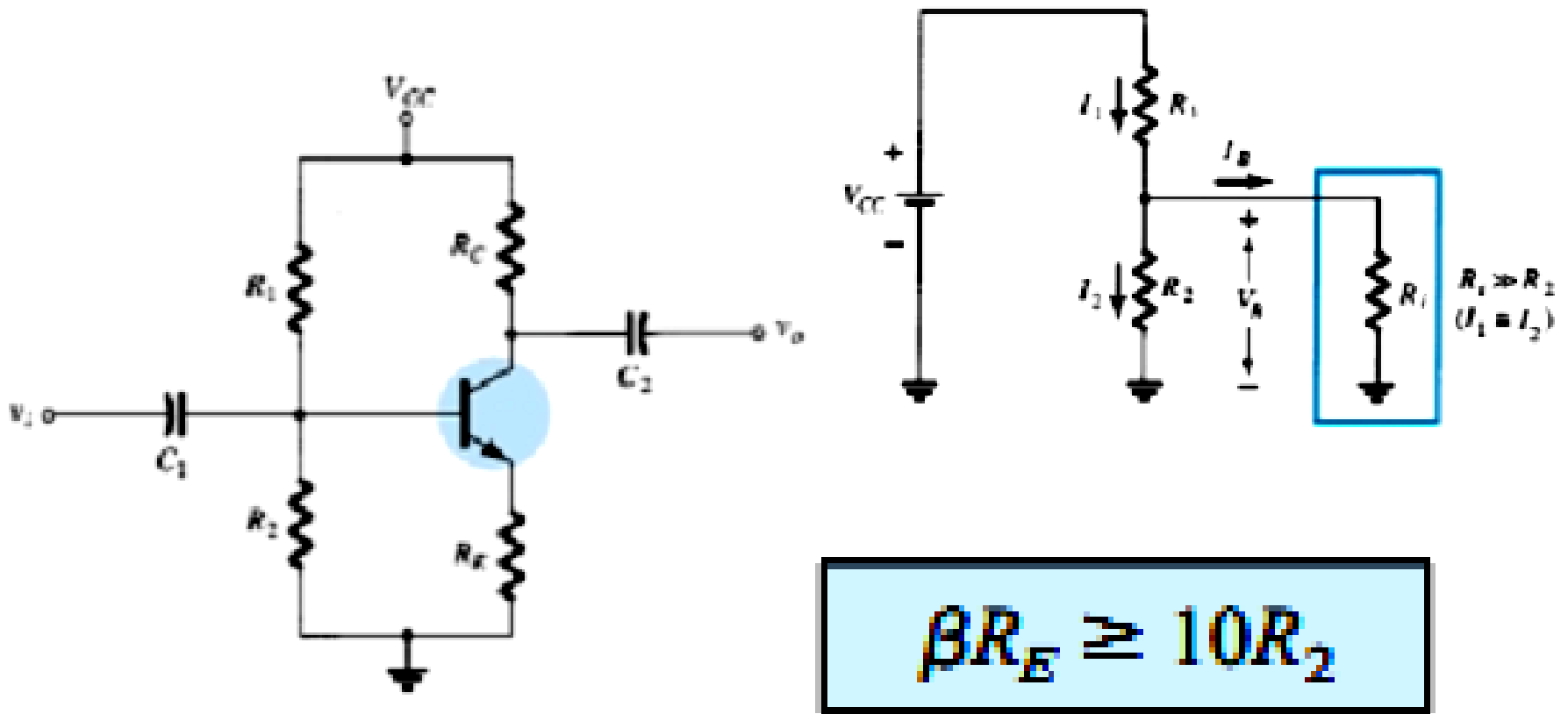

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$V_E = V_B - V_{BE}$$

$$I_E = \frac{V_E}{R_E}$$


$$I_{C_Q} \approx I_E$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$V_{CE_Q} = V_{CC} - I_C (R_C + R_E)$$

Problem:

- Determine I_C and V_{CE} .

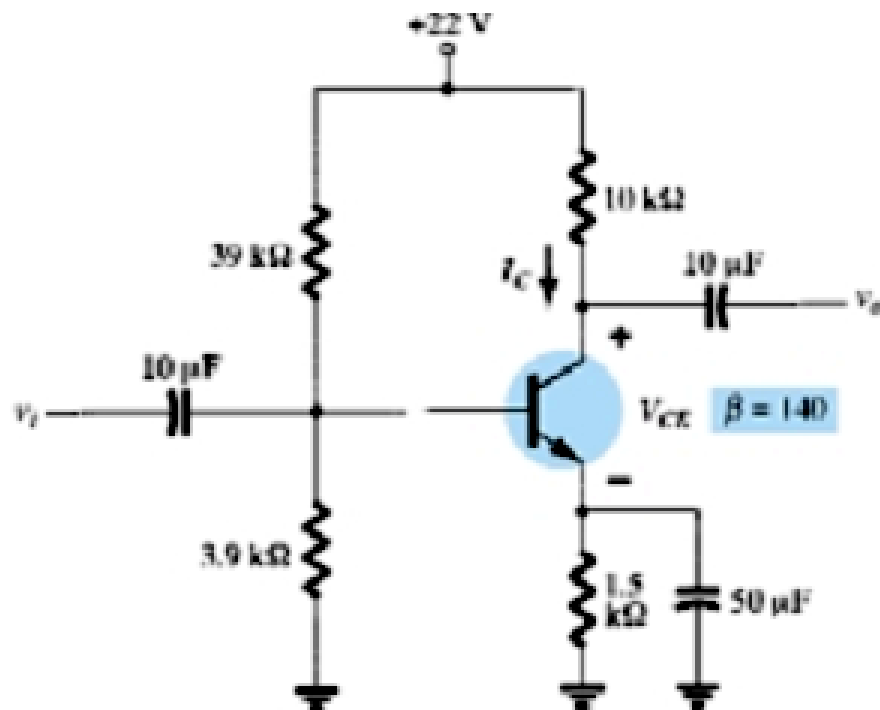

$$\beta R_E \geq 10 R_2$$

$$(140)(1.5 \text{ k}\Omega) \geq 10(3.9 \text{ k}\Omega)$$

$$210 \text{ k}\Omega \geq 39 \text{ k}\Omega \text{ (satisfied)}$$



$$\begin{aligned} V_B &= \frac{R_2 V_{CC}}{R_1 + R_2} \\ &= \frac{(3.9 \text{ k}\Omega)(22 \text{ V})}{39 \text{ k}\Omega + 3.9 \text{ k}\Omega} \\ &= 2 \text{ V} \end{aligned}$$

$$\begin{aligned}
 V_E &= V_B - V_{BE} \\
 &= 2 \text{ V} - 0.7 \text{ V} \\
 &= 1.3 \text{ V}
 \end{aligned}$$

$$I_{CQ} \approx I_E = \frac{V_E}{R_E} = \frac{1.3 \text{ V}}{1.5 \text{ k}\Omega} = \mathbf{0.867 \text{ mA}}$$

$$\begin{aligned}
 V_{CEQ} &= V_{CC} - I_C(R_C + R_E) \\
 &= 22 \text{ V} - (0.867 \text{ mA})(10 \text{ k}\Omega + 1.5 \text{ k}\Omega) \\
 &= 22 \text{ V} - 9.97 \text{ V} \\
 &= \mathbf{12.03 \text{ V}}
 \end{aligned}$$

DC Bias with Voltage Feedback

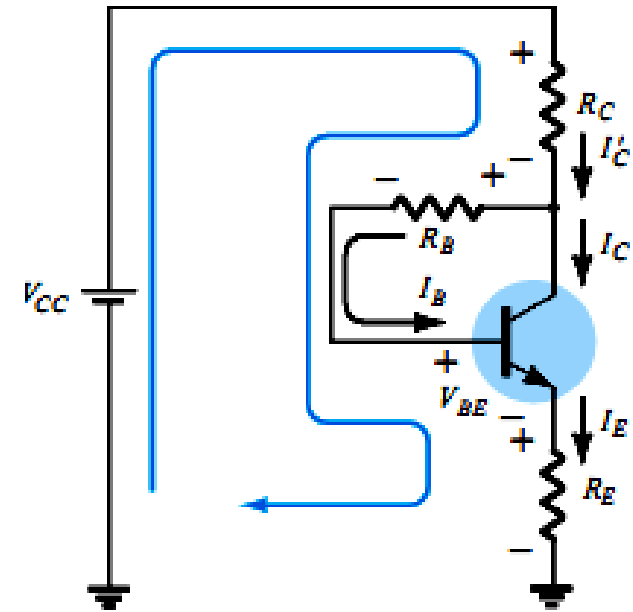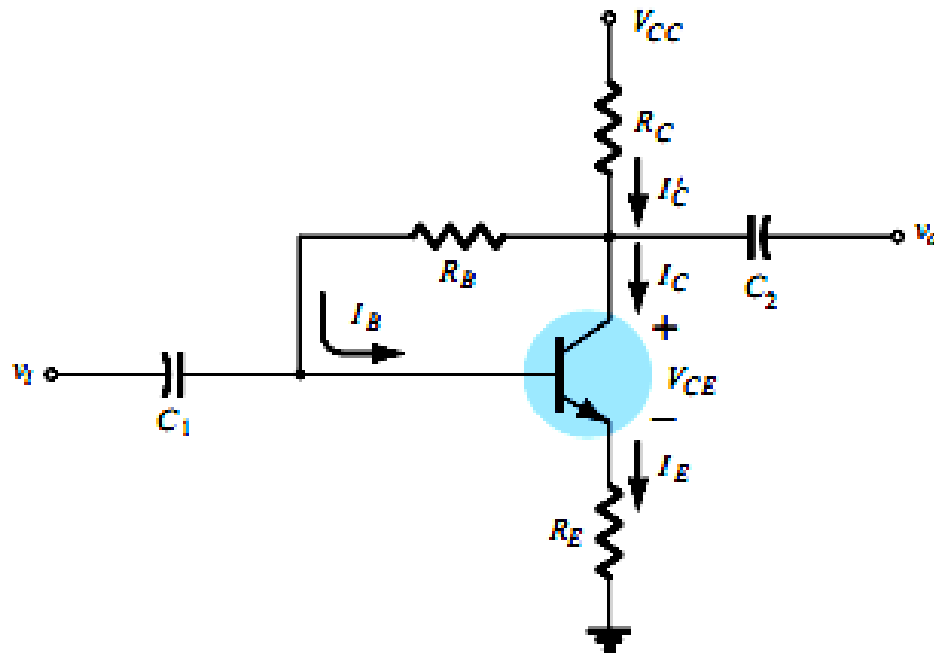


$$V_{CC} - I_C' R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$

Output Side

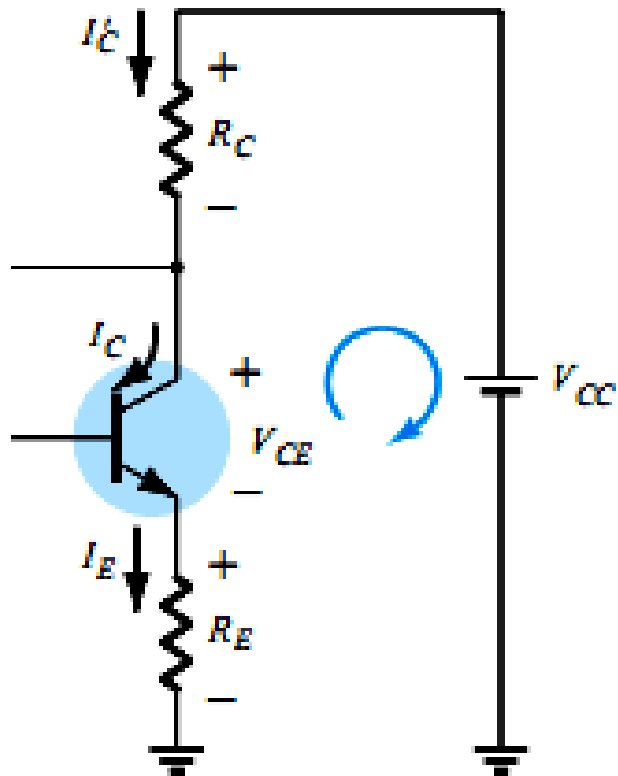

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

$$V_{CE} - V_{CC} + I_C(R_C + R_E) = 0$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

$$V_E = I_E R_E$$


$$V_{CE} = V_C - V_E$$

$$V_C = V_{CE} + V_E$$

$$V_C = V_{CC} - I_C R_C$$

Problem:

- Determine I_{CQ} and V_{CEQ} .

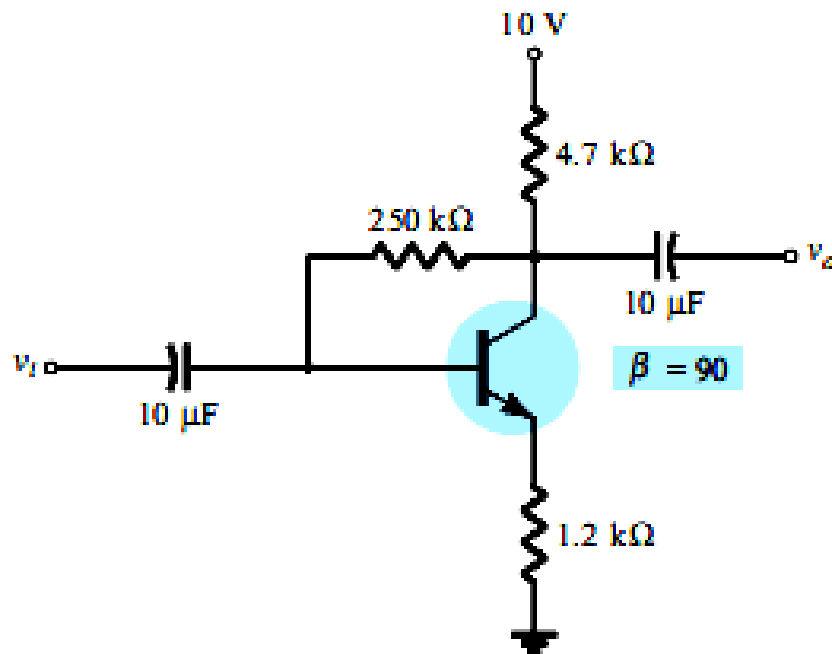

$$\begin{aligned} I_B &= \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)} \\ &= \frac{10 \text{ V} - 0.7 \text{ V}}{250 \text{ k}\Omega + (90)(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega)} \\ &= \frac{9.3 \text{ V}}{250 \text{ k}\Omega + 531 \text{ k}\Omega} = \frac{9.3 \text{ V}}{781 \text{ k}\Omega} \\ &= 11.91 \text{ }\mu\text{A} \end{aligned}$$


$$\begin{aligned} I_{CQ} &= \beta I_B = (90)(11.91 \text{ }\mu\text{A}) \\ &= 1.07 \text{ mA} \end{aligned}$$

$$\begin{aligned} V_{CEQ} &= V_{CC} - I_C(R_C + R_E) \\ &= 10 \text{ V} - (1.07 \text{ mA})(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega) \\ &= 10 \text{ V} - 6.31 \text{ V} \\ &= 3.69 \text{ V} \end{aligned}$$


Seatwork:

► Given $V_B = 4V$, determine:

- V_E
- I_C
- V_{CE}
- I_B

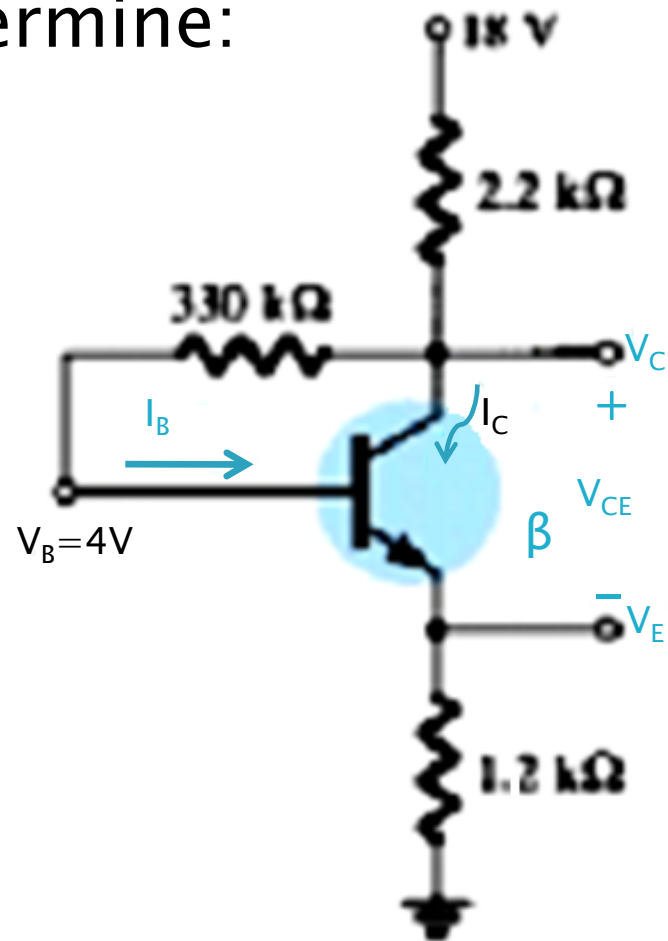

Common-Base Bias

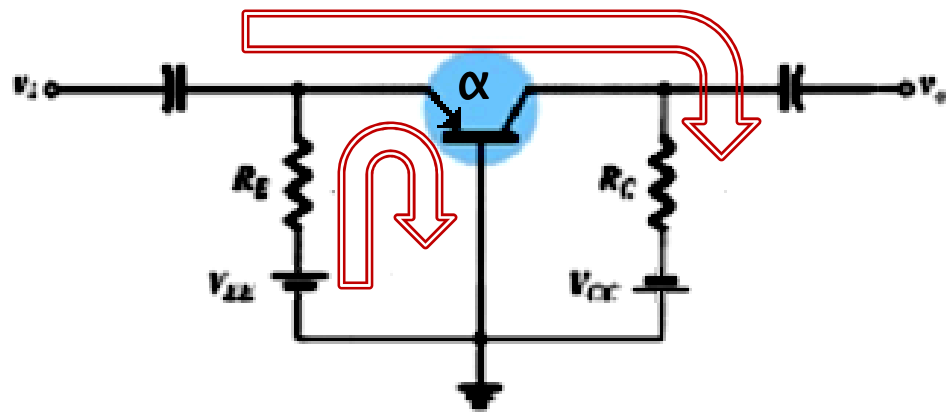

$$V_{EE} - I_E R_E - V_{EB} = 0$$


$$I_E = \frac{V_{EE} - V_{EB}}{R_E}$$

$$V_{EE} - I_E R_E - V_{EC} - I_C R_C + V_{CC} = 0$$

$$V_{EC} = V_{EE} + V_{CC} - I_E R_E - I_C R_C$$

Problem:

- Determine V_{CB} and I_B .

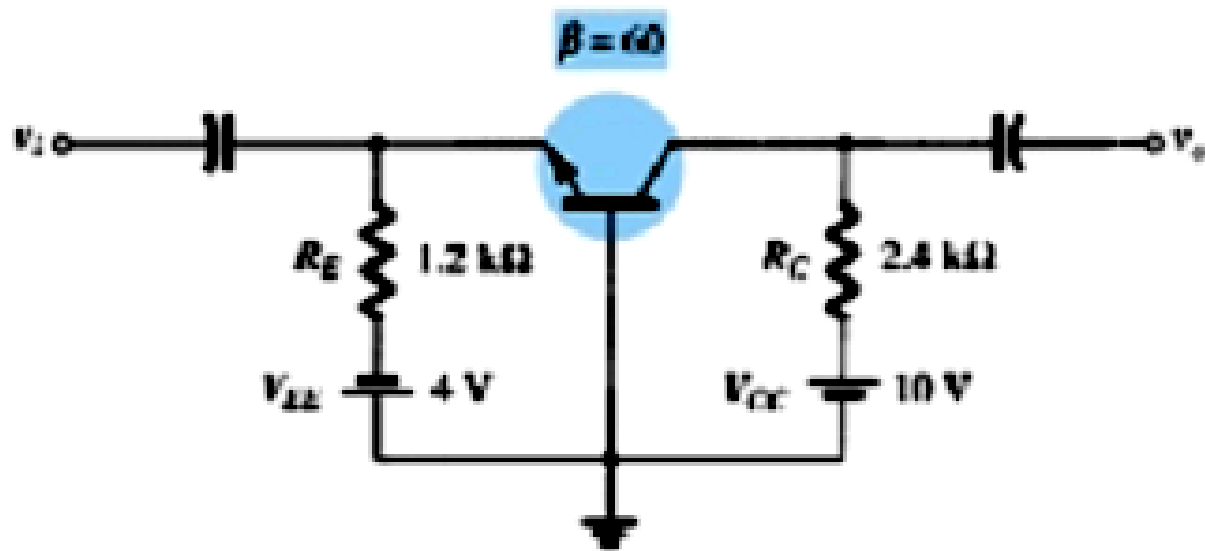

$$-V_{CB} + I_C R_C - V_{CC} = 0$$

$$\begin{aligned} V_{CB} &= V_{CC} - I_C R_C \text{ with } I_C \approx I_E \\ &= 10\text{ V} - (2.75\text{ mA})(2.4\text{ k}\Omega) \\ &= 3.4\text{ V} \end{aligned}$$

$$\begin{aligned} I_B &= \frac{I_C}{\beta} \\ &= \frac{2.75\text{ mA}}{60} \\ &= 45.8\text{ }\mu\text{A} \end{aligned}$$

$$-V_{EE} + I_E R_E + V_{BE} = 0$$

$$I_E = \frac{V_{EE} - V_{BE}}{R_E}$$

$$I_E = \frac{4\text{ V} - 0.7\text{ V}}{1.2\text{ k}\Omega} = 2.75\text{ mA}$$

Seatwork:

- Find V_C if $R_E = 1\text{ k}\Omega$, $R_C = 5\text{ k}\Omega$, $V_{EE} = 2\text{ V}$, $V_{CC} = 8\text{ V}$ and $\alpha = 0.98$.

